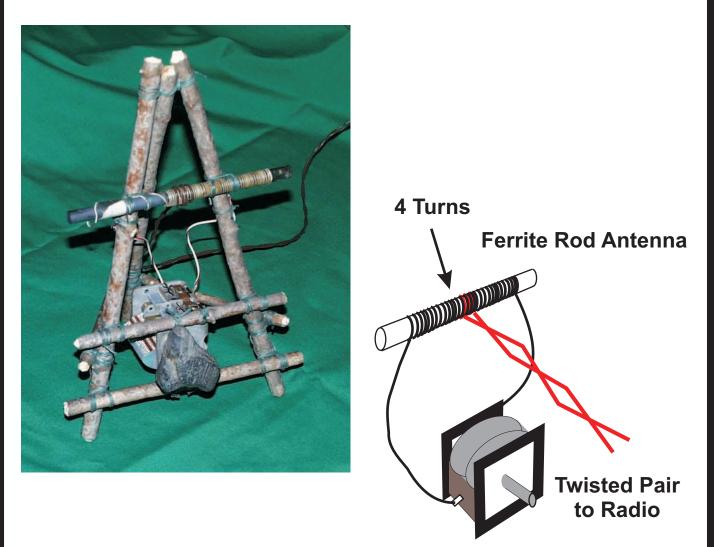
A Simple BCB Loop Antenna EVEN A CAVEMAN CAN DO IT!



Variable Capacitor

Use antenna rod and variable cap (approx. 365pF) from a 1950's table radio. Wrap four turns of hook-up wire around the center of rod. Twist leads (3-6 feet), and attach to antenna and ground terminals of your radio. If you're not up to wrap-it-twice-and-thrap-it-thrice, mount it on plywood, a cigar box, Lego or what have you.

Al Klase - N3FRQ 2007